

Fomenky's

UNIVERSITY OF BUEA

COLLEGE OF TECHNOLOGY

MONTH: August

SECOND SEMESTER EXAMINATIONS

TIME ALLOWED: 2h

COURSE INSTRUCTORS: TCHINDA, NJITACKE, MEGAM, ATEUFACK

DATE: 06 Aug. 2020

COURSE CODE: EEC 302

COURSE TITLE: Digital Electronic Laboratory

DESIGN AND IMPLEMENTATION OF a 2 – bit MAGNITUDE COMPARATOR

THEORY:

Comparing two numbers is an operation which aims to determine if one number is greater than, less than (or) equal to the other number. A magnitude comparator is a combinational circuit that compares two numbers A and B and determine their relative magnitude. The outcome of the comparator is specified by two binary variables that indicate whether $A > B$, $A = B$ (or) $A < B$.

Table 1. Truth table of the comparator

A1	A0	B1	B0	$A > B$	$A = B$	$A < B$
0	0	0	0			
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0			
0	1	1	1			
1	0	0	0			
1	0	0	1			
1	0	1	0			
1	0	1	1			
1	1	0	0			
1	1	0	1			
1	1	1	0			
1	1	1	1			

Components Required : IC 7404, IC 4030, IC 4081, IC 4071, IC 4073, resistor, Leds, logictoggle.

- 1- Give the aim of this experiment.
- 2- Realize the diagram of Figure 1 in Proteus Software.
- 3- Using proteus simulation, fill Table 1
- 4- Draw the Karnaugh-map (K-map) of each output obtained in Table1
- 5- Write the logic equation of the following output:
 - a- $A=B$
 - b- $A>B$
 - c- $A<B$

