

Quick test no.1

EEEC207: Circuit Analysis


Duration: 15mn

Name: Fomenky Folefac Nka-FolepMatricule: CT17A016

NB on MCQ questions: read the questions carefully and mark an X only on the letter of the correct answer.

- One millivolt is one millionth of a volt. (a) True (b) ☒ False
- The unit of current is: (a) coulomb (b) ☒ ampere (c) volt (d) joule
- A 4-A current charging a dielectric material will accumulate a charge of 24 C after 6 s. (a) ☒ True (b) False
- The dependent source in the figure beside is:

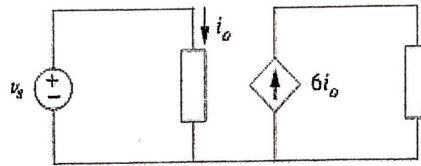- (a) ☒ voltage-controlled current source
 (b) voltage-controlled voltage source
 (c) current-controlled voltage source
 (d) current-controlled current source



- In some circuit element the power is 20 W and the voltage is 10 V. How much current flows?

$$P = 20W, V = 10V, I = ?$$

$$\text{But } P = IV \text{ and } I = \frac{P}{V}$$

$$\Rightarrow I = \frac{20}{10} = 2A \quad \underline{I = 2A}$$

- A flashlight battery has a rating of 0.8 ampere-hours (Ah) and a lifetime of 10 hours.

(a) How much current can it deliver? (b) How much power can it give if its terminal voltage is 6 V? (c) How much energy is stored in the battery in Wh?

$$Q = 0.8Ah$$

$$t = 10h$$

$$I = \frac{Q}{t} = \frac{0.8Ah}{10} = 0.08A$$

$$P = 0.8Ah$$

$$\text{rating} = 0$$


$$t = 10 \text{ hours}$$

$$b) P = IV, V = 6V, I = 0.08A$$

$$P = 0.08 \times 6$$

$$P = 0.48W$$

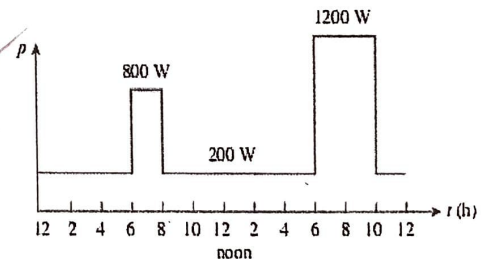- Figure beside shows the power consumption of a certain household in 1 day. Calculate: (a) the total energy consumed in kWh, (b) the average power per hour over the total 24 hour period.



- Find I and the power absorbed by each element in the network below:

