

## Quick test no.2

EEC207: Circuit Analysis / EEC223: Fundamentals of Electrical Engineering

Duration: 20mn

Name: Fomenky Folefac Nka-FolefacMatricule: ET17016

NB on MCQ questions: read the questions carefully and mark an X only on the letter of the correct answer.

1. An electric heater draws 10 A from a 120-V line. The resistance of the heater is:

- (a) 1200  $\Omega$  (b) 120  $\Omega$  (c) ☒ 12  $\Omega$  (d) 1.2  $\Omega$

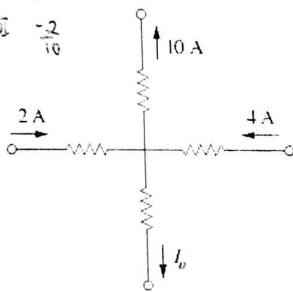
2. The current  $I_o$  in the figure 1 is: (a) ☒ -4 A (b) -2 A (c) 4 A (d) 16 A3. The current  $I$  in the figure 2 is: (a) -0.8 A (b) ☒ -0.2 A (c) 0.2 A (d) 0.8 A4. In the circuit in figure 3,  $V$  is: (a) 30 V (b) 14 V (c) 10 V (d) ☒ 6 V

Figure 1

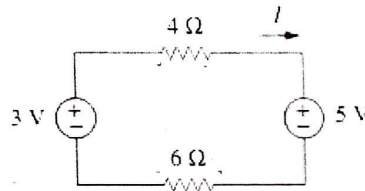


Figure 2

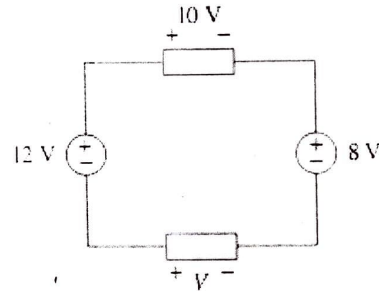
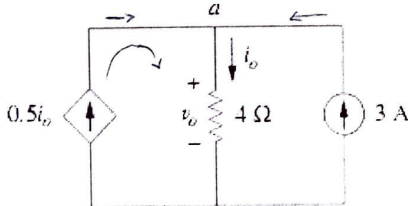


Figure 3

5. Ohm's law states that the voltage  $V$  across a resistor is directly proportional to the current flowing through the resistor. (a) ☒ True (b) False6. Find the current  $i_o$  and the voltage  $v_o$  in the circuit below.

from KCL  
 $0.5 i_o = 3 + i_o$   
 $i_o - 0.5 i_o = 3A$   
 $0.5 i_o = 3A$   
 $i_o = 6A$   
from ohm's law  
 $V_o = 4(i_o)$   
 $= 4(6)$   
 $V_o = 24V$

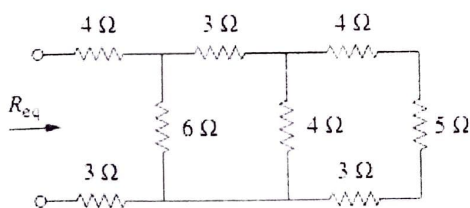
7. By combining the resistors in the figure a, find  $R_{eq}$ .

Figure a

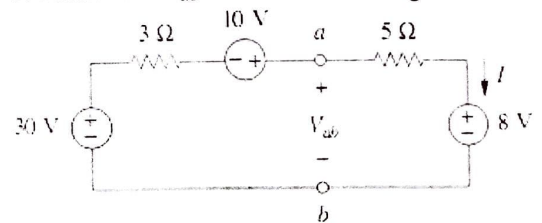
8. Find  $I$  and  $V_{ab}$  in the circuit of figure b

Figure b